


## Digital Logic Trainer board

Model: LT-609

Brand: L-TEK

Country of origin China

Assembly by LabTech

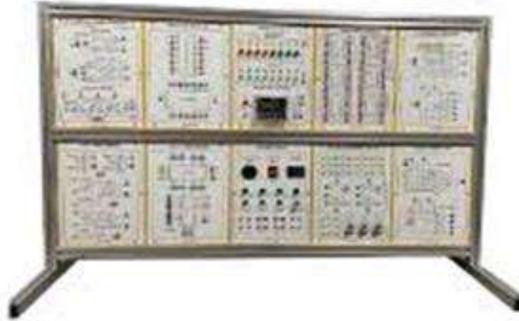

### Description:

The Digital Logic Trainer board should consist of below:

The whole trainer is fully designed by FPGA/CPLD logic circuit. Buffer circuits have enhanced protection for each module which is powered by main unit through power socket, avoiding wrong input power source during the experiment. Covers different levels of logic circuit experiments, ranging from combinational logic, sequential logic as well as the logic circuit interfacing with microcontroller and practical application circuit for daily use. Includes various types of ADC & DAC circuits to learn different interfacing circuits between analog and digital signal. Built-in 8- channel multiplexer in main unit to measure multiple digital signals in real time. Multiple operation modes from 4-digit 7-segment display (a) scanning display mode, (b) individual digit display mode, (c) frequency counter mode for measurement of internal and external clock. Individual keep case for all modules for easy storing and carrying.

Main Unit:

DC Power Supply

Fixed DC power supply: +5V/2A, -5V/0.5A, +12V/2A With  
overload protection

Clock Generator

Signal amplitude output: 3.3V

With adjustable output frequency: square wave, 1Hz ~  
1MHz, 6 range

Frequency display :4-digit, 7-segment LED

Logic Level Switch: Toggle switches x 8, 3.3V output Data Level

Switch: 8-bit DIP switch x 2, 3.3V output Pulse Signal Generator

2 sets of toggle switch with independent control output, Each set with Q, Q' output Pulse width > 5ms, each with Denounce circuit

Logic Level Indicator

16-bit LED with driver and protection circuit Input

Impedance: > 100K ohms

8 Channel Logic Signal Tracer

8 logic signal input: input impedance:  $\geq 100K$  ohms, 3.3V input Fixed DC

level shift for each channel

Input signal attenuation ratio: 1/8 Output

signal: BNC or 2mm plug

Oscilloscope SYNC. select: ALT/CHOP and scan-frequency adjustment The function can be used only with analog oscilloscope

7-segment LED display & frequency measurement DIP

switches select the function:

00: Scanning display mode

Common anode for the control of 7-segments a ~ g Scanning

cathode for the control of 4-digit S0 ~ S3 Independent display mode

Input 4-digit of data individually and decode the data at

7-segment display separately

Independent binary input and hexadecimal output 10:

Frequency counter for internal clock

Display the frequency of clock generator from main unit Frequency range:

0.001KHz ~ 999.9KHz

11: Frequency counter for external clock

Display the frequency of clock signal from external unit Frequency range:

0.001KHz ~ 999.9KHz

Rotary Encoder Rotary encoder output: PA, PB and GND signal, 3.3V output Standard Signal

Generator 5 sets of frequency:

20MHz, 1MHz, 10KHz, 100Hz, 1Hz

Experiment Modules

All built-in DC power socket module supply DC power from the main unit.

Each module includes a CPLD chip to implement all digital circuits shown on module panel. 2mm

sockets, bridge plugs, and cables are used throughout all modules so that students can easily create the



circuits and compare different results in short time.

With comprehensive experiment manual.

List of Modules

Combinational Logic Circuit Experiment

Arithmetical Logic/Tri-state & Code Converter Experiment Encoder,

Decoder & Multiplexer Logic Circuit Experiment Flip-flop &

Sequential Logic & Counter Circuit Experiment Oscillator/Pulser; Load;

Up/Down Counter Circuit Experiment

Memory; Matrix LED; DAC/ADC & MCU Interface Circuit Experiment Digital &

Analog Timer, Pulse Generator Circuit Experiment

Ramp-compare/SAR/Dual-slope ADC Experiment Keyboard &

Display for Stepping Motor Position Control Precise Digital Clock

Timer

Universal CPLD & Breadboard Experiment List of Experiments

Combinational Logic Circuit Experiment

NOR gate circuit NAND gate

circuit XOR gate circuit

Constructing XOR gate with NAND gate The

combination with basic gates

AND-OR-INVERTER (A-O-I) gate circuit Comparator

circuit

Comparator constructed with basic logic gates

Comparator constructed with TTL IC

Schmitt gate circuit

Open-collector gate circuit High

voltage/current circuit

Constructing an AND gate with open collector gate

Half-adder and full-adder circuit Construct HA with basic logic gates

Half-sub tractor and full-sub tractor circuit Subtract or circuit constructed with basic logic gates Bit

parity generator circuit Bit parity generator constructed with XOR gates

Constructing a 4-to-10 decoder with TTL IC

The switch characteristics of TTL level conversion circuit Arithmetical

Logic/Tri-state & Code Converter Experiment CMOS FET tractate gate

circuit



Truth table measurements  
Constructing an AND gate with tractate gate  
Bidirectional transmission circuit  
Half-adder and full-adder circuit Full-adder  
circuit with IC  
High-speed adder carry generator circuit  
BCD code adder circuit  
Half-sub tractor and full-sub tractor circuit Full adder and inverter circuit Arithmetic  
Logic Unit (ALU) circuit  
Bit parity generator circuit Bit parity generator IC Hex to  
Dec/Dec to Hex digital conversion  
8-digit Dec-to-Hex conversion 8-bit Hex-  
to-Dec conversion  
Encoder, Decoder & Multiplexer Logic Circuit Experiment Encoder  
circuit  
Constructing a 4-to-2 encoder with basic gates Constructing  
a 9-to-4 encoder with TTL IC Decoder circuit  
Constructing a 2-to-4 decoder with basic gates BCD-to-  
7-segment decoder  
DE multiplexer circuit Constructing a 2-output DE multiplexer with  
basic logic gates  
Digitally controlled analog multiplexer/ DE multiplexer circuit The  
switch characteristics of CMOS level conversion circuit Flip-flop &  
Sequential Logic & Counter Circuit Experiment Flip-flop circuits  
Construct R-S flip-flop with basic logic gates Construct  
D flip-flop with R-S flip-flops  
Construct noise elimination circuit with R-S flip-flops Construct J-  
K flip-flop with D flip-flops  
The J-K flip-flop of delay and differential  
Construct master-slave J-K flip-flops with dual R-S flip-flops Construct  
shift register with D flip-flops  
Preset left/right shift register J-K flip-  
flop counters  
Asynchronous binary up counter Asynchronous



binary down counter Asynchronous decade up  
counter Synchronous binary counter Synchronous  
binary up counter Synchronous binary up/down  
counter Johnson counter  
Ring counter  
Oscillator/Pulsar; Load; Up/Down Counter Circuit Experiment  
Constructing Random Access Memory (RAM) with D flip-flop 64-bit  
Random Access Memory (RAM) circuit  
Erasable Programmable Read Only Memory (EPROM) circuit  
Asynchronous four-bit binary up counter (use of 7493 IC) Presentable  
binary up/down counter  
Presentable decimal up/down counter  
Construct non-retrigger able circuit with the specialized CMOS IC Construct  
retrigger able circuit with CMOS IC  
Construct a variable duty cycle oscillator circuit with dual constable multivibrators Memory,  
Matrix LED & DAC/ADC & MCU Interface Circuit Experiment Electronic EPROM  
(EEPROM) circuit  
DAC0800 unipolar conversion circuit experiments Bipolar  
output conversion circuit  
ADC0804 8-bit SAC analog-to-digital converter experiment Constructing  
dynamic scanning counter with single Chip microprocessor  
Digital & Analog Timer, Pulse Generator Circuit Experiment  
Constructing oscillator circuit with basic logic gates Resistor-  
capacitor multivibrator  
Resistor-capacitor crystal multi vibrator Constructing  
oscillator circuit with Schmitt gate Resistor-capacitor  
oscillator  
Variable duty cycle resistor-capacitor oscillator 555 IC  
oscillator circuit  
555 oscillator circuit  
Voltage controlled oscillator circuit Mon  
stable multi vibrator circuits  
Low-speed monostable multivibrator circuits Mon  
stable ON/OFF delay circuit Mono stable ON/OFF



timer circuit

Construct mono stable multi vibrator circuit with 555 IC

Numerically-Controlled Oscillator (NCO) signal generator Precise-frequency function generator

Variable-duty-cycle NCO signal generator

Variable-ON/OFF delay and difference control experiments Precise

15-bit symmetric/asymmetric PWM generator Ramp-compare/SAR/Dual-slope ADC Experiment

Simple R-2R unipolar output D/A converter experiments 8-bit digital-ramp A/D converter experiment

8-bit successive-approximation A/D converter experiment 8-bit dual-slope A/D converter experiment

Keyboard & Display for Stepping Motor Position Control Stepper motor position/speed control experiment

Precise Digital Clock Timer Clock experiment

Timer experiment

Universal CPLD & Breadboard Experiment Create block diagram/schematic file in QUARTUS 16-bit Hex counter

16-bit decimal counter

16-bit presetable decimal up/down counter

16-bit scanning controller for 7-segment display

16-bit up/down counter and its indication by a 7-segment display

Electronic music box

The traffic light with animation and time indication Equipment

Required

Hand-held Digital Multi meter

Digital Storage Oscilloscope (DSO) : 100MHz bandwidth, 1GS/s sampling rate and FFT function or better.

Accessories: Connecting Wire: 2 set, User Manual: 2 Nos, Standard Accessories

Warranty: 1 (One) year with services

